

# **BASIC ELECTRONICS ENGINEERING**

**(RBL1B002)**

***MODULE-1***

BJT = *Bipolar Junction Transistor*




*Transistor = Transfer + Resistor*

# BIPOLAR JUNCTION TRANSISTOR (BJT)



- The transistor is a three layer semiconductor device consisting of either two N-type & one P-type or two P-type & one N-type semiconductor.
- It has three terminals
  - Base (B)
  - Emitter (E)
  - Collector (C)
- In this device both electrons & holes take part in the conduction. Hence it is called as *bipolar*.

# STRUCTURE & SYMBOL OF BJT

**N P N**

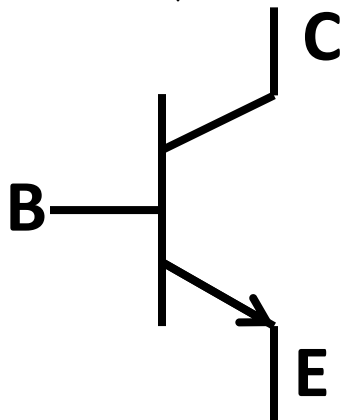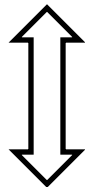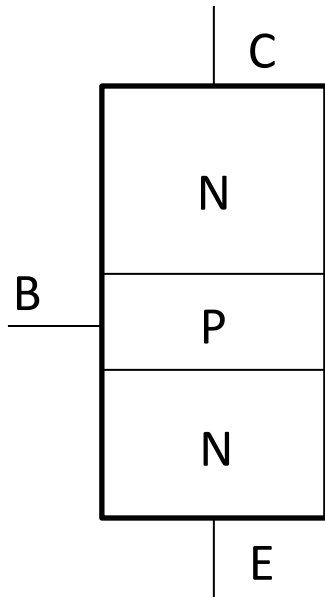

**P N P**

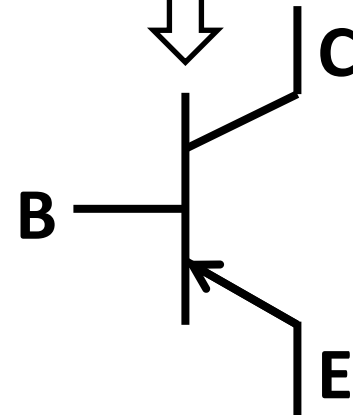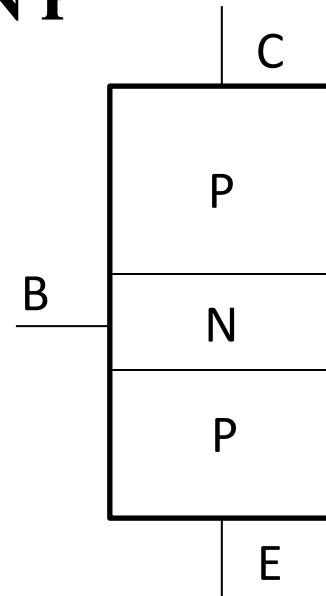

# **TERMINALS**

## **1. EMITTER**

- The main function of the emitter terminal is to supply the majority charge carriers to the base.
- For NPN type BJT the majority charge carriers are electrons & for PNP type BJT the majority charge carriers are holes.
- The emitter is always heavily doped.

## **2. BASE**

- The base is a thin layer and it is lightly doped. It's main function is to pass the majority charge carriers to the collector.

### **3. COLLECTOR**


- The main function of the collector is to collect the majority charge carriers coming from the base.
- It is moderately doped.

## **TRANSISTOR CONFIGURATION**

- The BJT can be connected in circuit in 3 different configurations:
  - Common Base (CB)
  - Common Emitter (CE)
  - Common Collector (CC)

# Common Base (CB)

## PNP Type

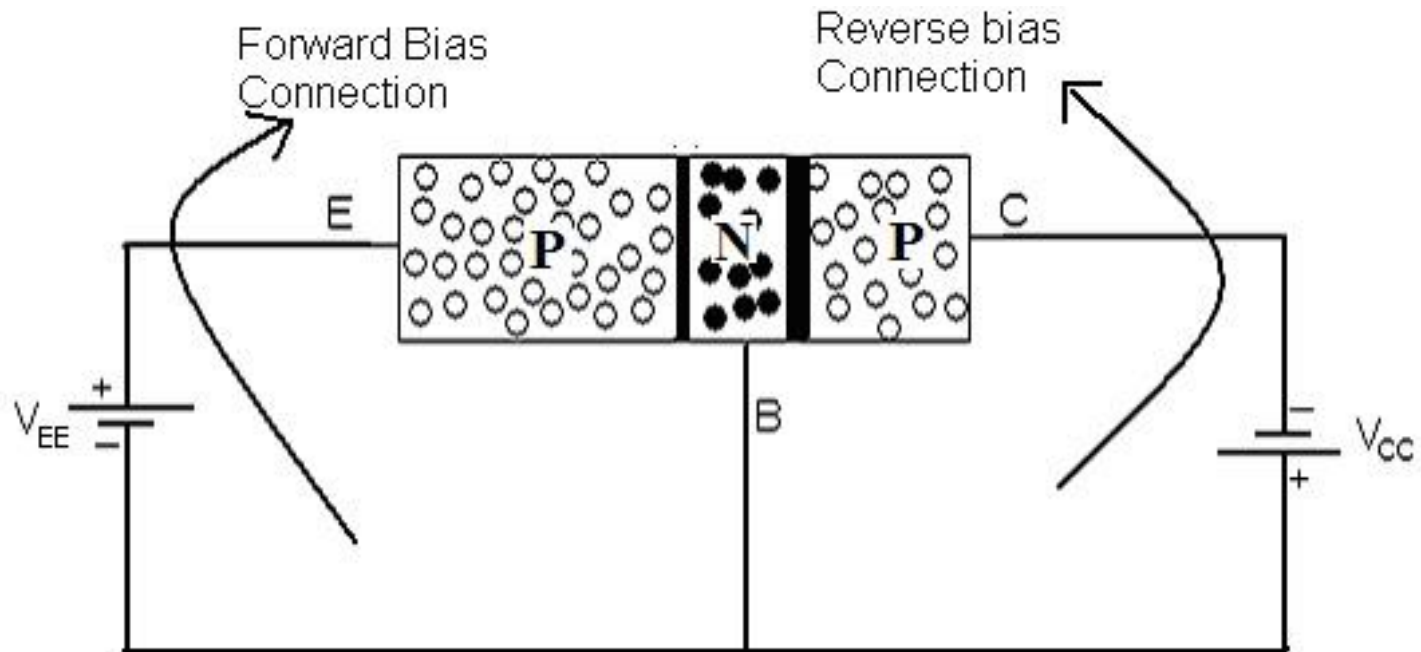


- For the Operation of the transistor, the Emitter – Base junction must be forward bias and Collector – Base junction must be reverse bias.
- The forward bias at the emitter terminal will repel the holes from emitter side towards the base constituting emitter current ( $I_E$ ).
- As the base is lightly doped, some of the holes will recombine with electron and rest of holes will enter the collector.
- Due to this, a current at the base is observed which is called as base current ( $I_B$ ).
- The holes entering into the collector will constitute collector current ( $I_C$ ).
- Hence the majority carriers from emitter travels to the collector through the base.
- Hence,  $I_E = I_B + I_C$



# Common Base (CB)

## NPN Type

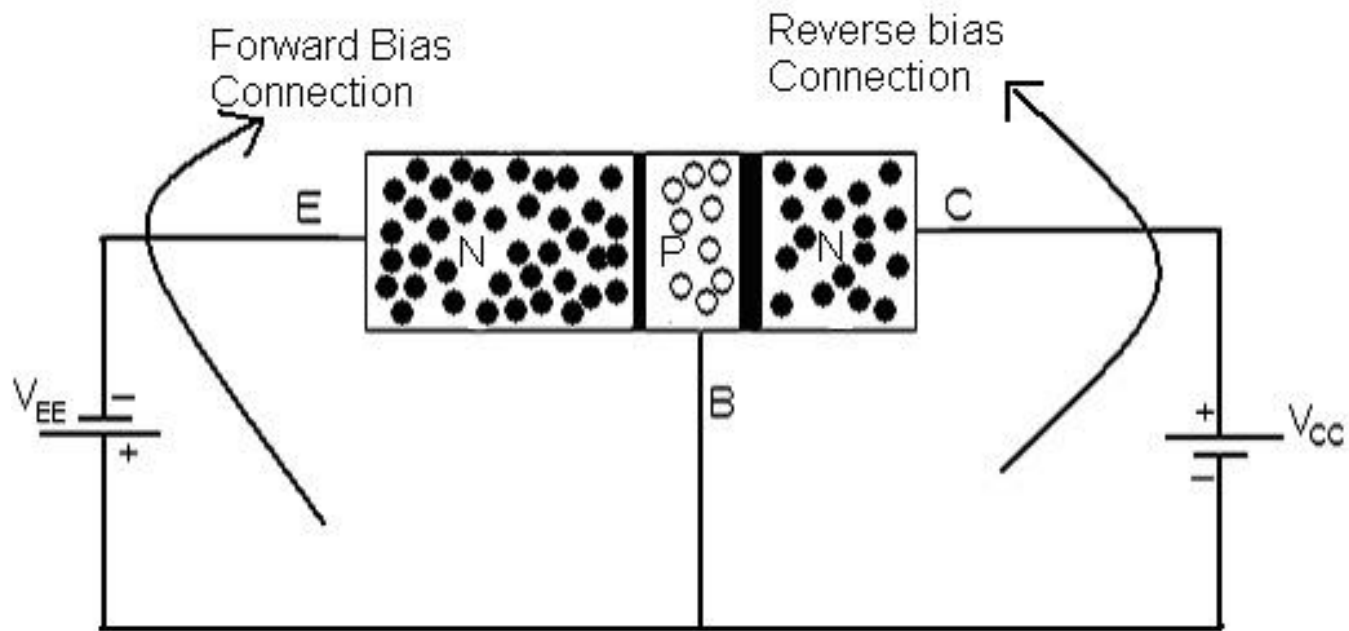

- For the Operation of the transistor, the Emitter – Base junction must be forward bias and Collector – Base junction must be reverse bias.
- The forward bias at the emitter terminal will repel the electrons from emitter side towards the base constituting emitter current ( $I_E$ ).
- As the base is lightly doped, some of the electrons will recombine with holes and rest of electrons will enter the collector.
- Due to this, a current at the base is observed which is called as base current ( $I_B$ ).
- The electrons entering into the collector will constitute collector current ( $I_C$ ).
- Hence the majority carriers from emitter travels to the collector through the base.
- Hence,  $I_E = I_B + I_C$

## **Current Amplification Factor ( $\alpha$ )**

It is the ratio of collector current to the emitter current at constant collector base voltage.

$$\text{i.e. } \alpha = \left. \frac{I_C}{I_E} \right|_{V_{CB}=\text{Constant}}$$

## **Collector Current ( $I_C$ )**

The collector current consists of:

1. The part of emitter current which reaches from the emitter and is given by

$$I_C = \alpha \cdot I_E$$

2. The leakage current due to the flow of minority carrier across CB junction and is given by  $I_{CBO}$

Hence the total collector current is given by

$$I_C = \alpha \cdot I_E + I_{CBO}$$


$$\Rightarrow I_C = \alpha(I_B + I_C) + I_{CBO}$$

$$\Rightarrow I_C(1 - \alpha) = \alpha I_B + I_{CBO}$$

$$\Rightarrow I_C = \frac{\alpha}{1-\alpha} I_B + \frac{1}{1-\alpha} I_{CBO}$$

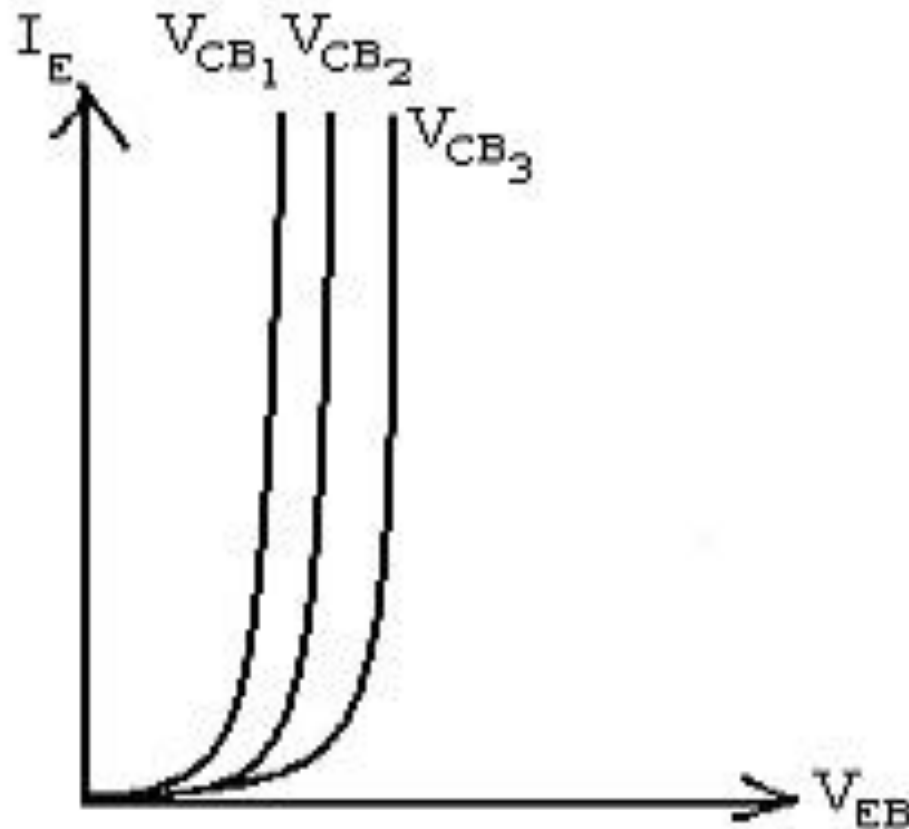
## Input VI Characteristics

It is the curve between the current  $I_E$  and voltage  $V_{EB}$  at constant collector base voltage  $V_{CB}$ .



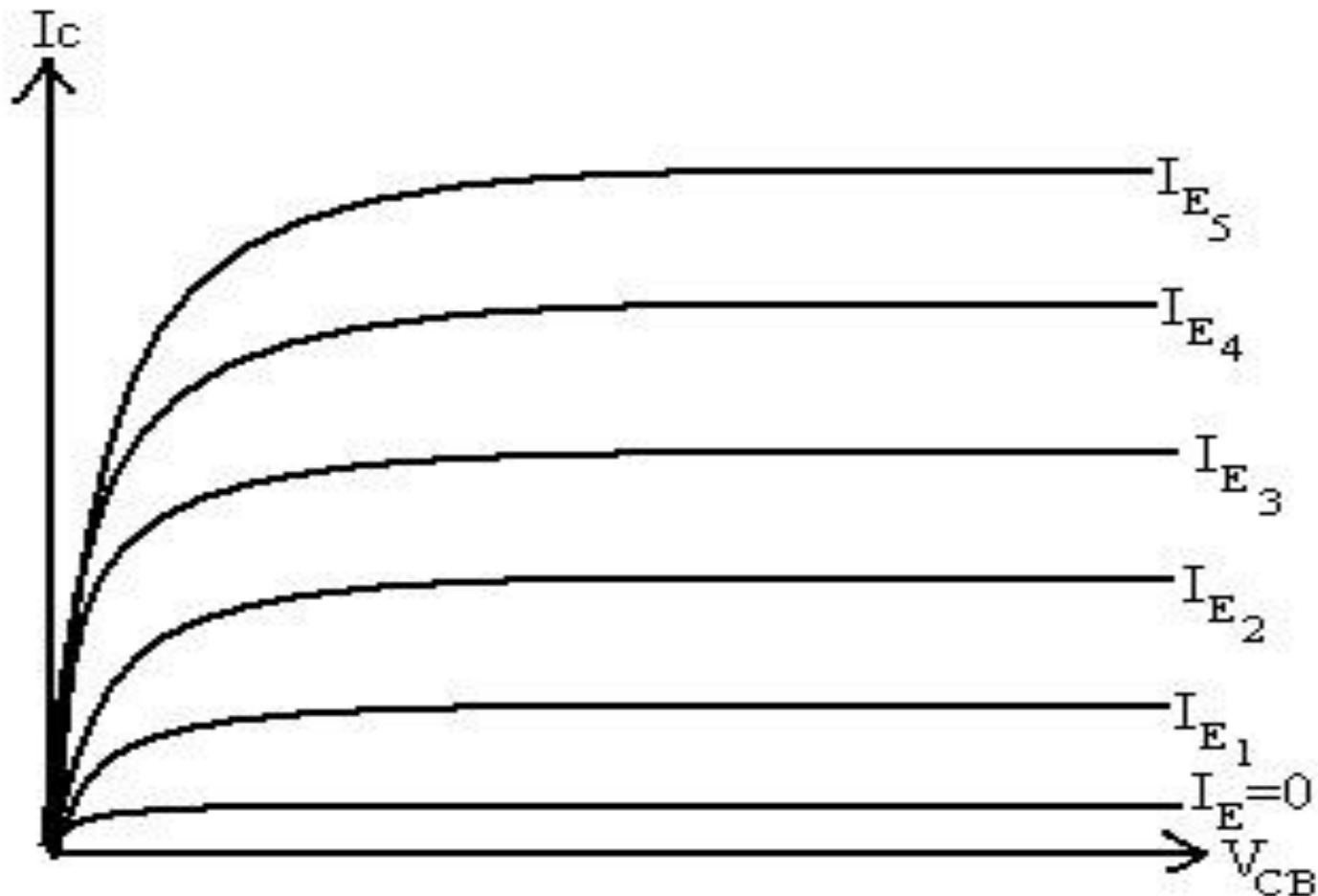
# Output VI Characteristics

It is the curve between the current  $I_C$  and voltage  $V_{CB}$  at constant collector base voltage  $I_E$ .



# Common Emitter (CE)

## PNP Type

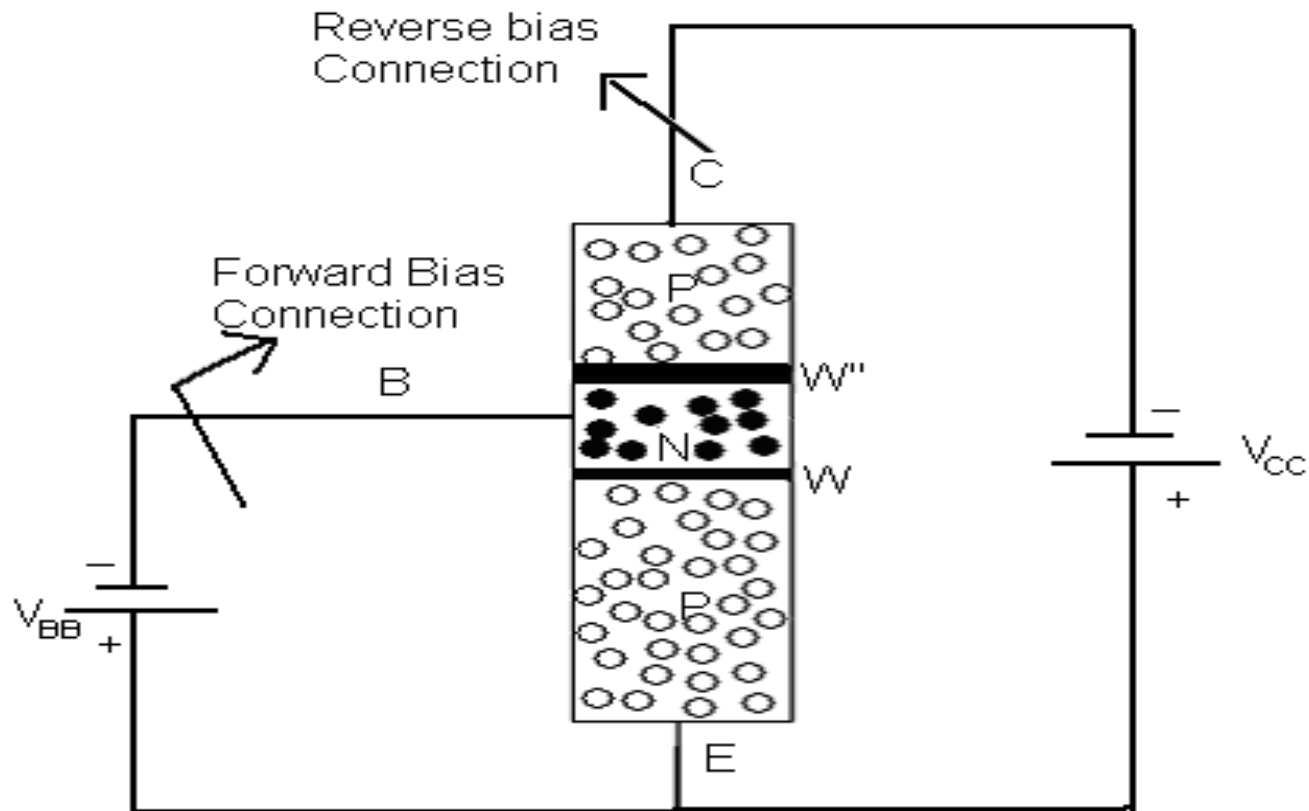


- For the Operation of the transistor, the Base –Emitter junction must be forward bias and Collector –Emitter junction must be reverse bias.
- The forward bias at the emitter terminal will repel the holes from emitter side towards the base constituting emitter current ( $I_E$ ).
- As the base is lightly doped, some of the holes will recombine with electron and rest of holes will enter the collector.
- Due to this, a current at the base is observed which is called as base current ( $I_B$ ).
- The holes entering into the collector will constitute collector current ( $I_C$ ).
- Hence the majority carriers from emitter travels to the collector through the base.
- Hence,  $I_E = I_B + I_C$



# Common Emitter (CE)

## NPN Type

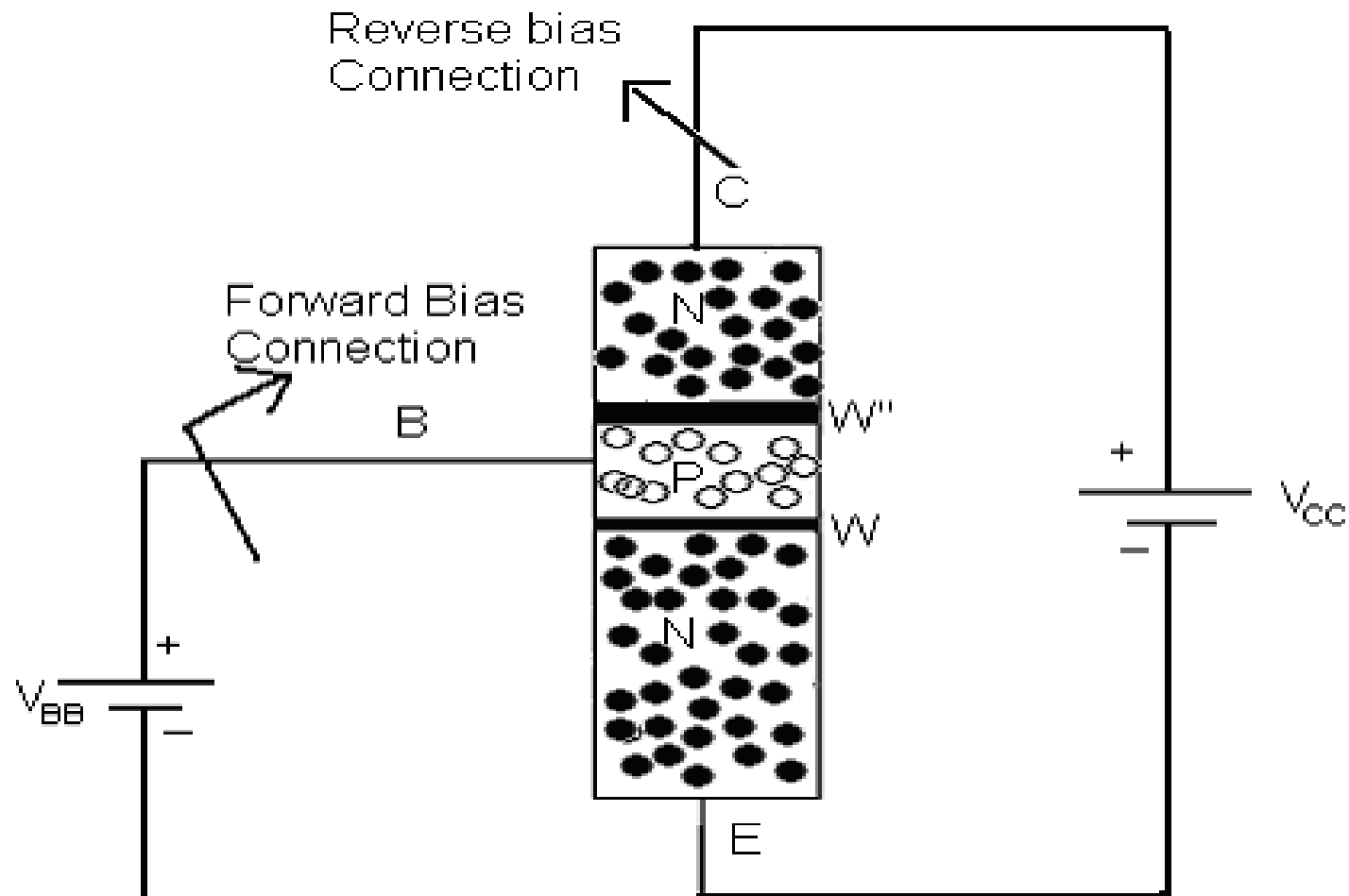

- For the Operation of the transistor, the Base –Emitter junction must be forward bias and Collector –Emitter junction must be reverse bias.
- The forward bias at the emitter terminal will repel the electrons from emitter side towards the base constituting emitter current ( $I_E$ ).
- As the base is lightly doped, some of the electrons will recombine with holes and rest of electrons will enter the collector.
- Due to this, a current at the base is observed which is called as base current ( $I_B$ ).
- The electrons entering into the collector will constitute collector current ( $I_C$ ).
- Hence the majority carriers from emitter travels to the collector through the base.
- Hence,  $I_E = I_B + I_C$

## Current Amplification Factor ( $\beta$ )

It is the ratio of collector current to the base current at constant collector emitter voltage.

$$\text{i.e. } \beta = \left. \frac{I_C}{I_B} \right|_{V_{CE}=\text{Constant}}$$

*# The relation between  $\alpha$  &  $\beta$ .*

$$\beta = \frac{I_C}{I_B} = \frac{I_C}{I_E - I_C} = \frac{I_C / I_E}{I_E / I_E - I_C / I_E} = \frac{\alpha}{1 - \alpha}$$

## Collector Current ( $I_C$ )

We know that,

$$I_C = \frac{\alpha}{1 - \alpha} I_B + \frac{1}{1 - \alpha} I_{CBO}$$

When  $I_B = 0$ , i.e. base is open, the collector current will be the current across the emitter & is represented as

$I_{CEO}$ .


$$\therefore I_{CEO} = \frac{1}{1 - \alpha} I_{CBO}$$

So,

$$\begin{aligned} I_C &= \frac{\alpha}{1 - \alpha} I_B + I_{CEO} \\ \Rightarrow I_C &= \beta I_B + I_{CEO} \end{aligned}$$
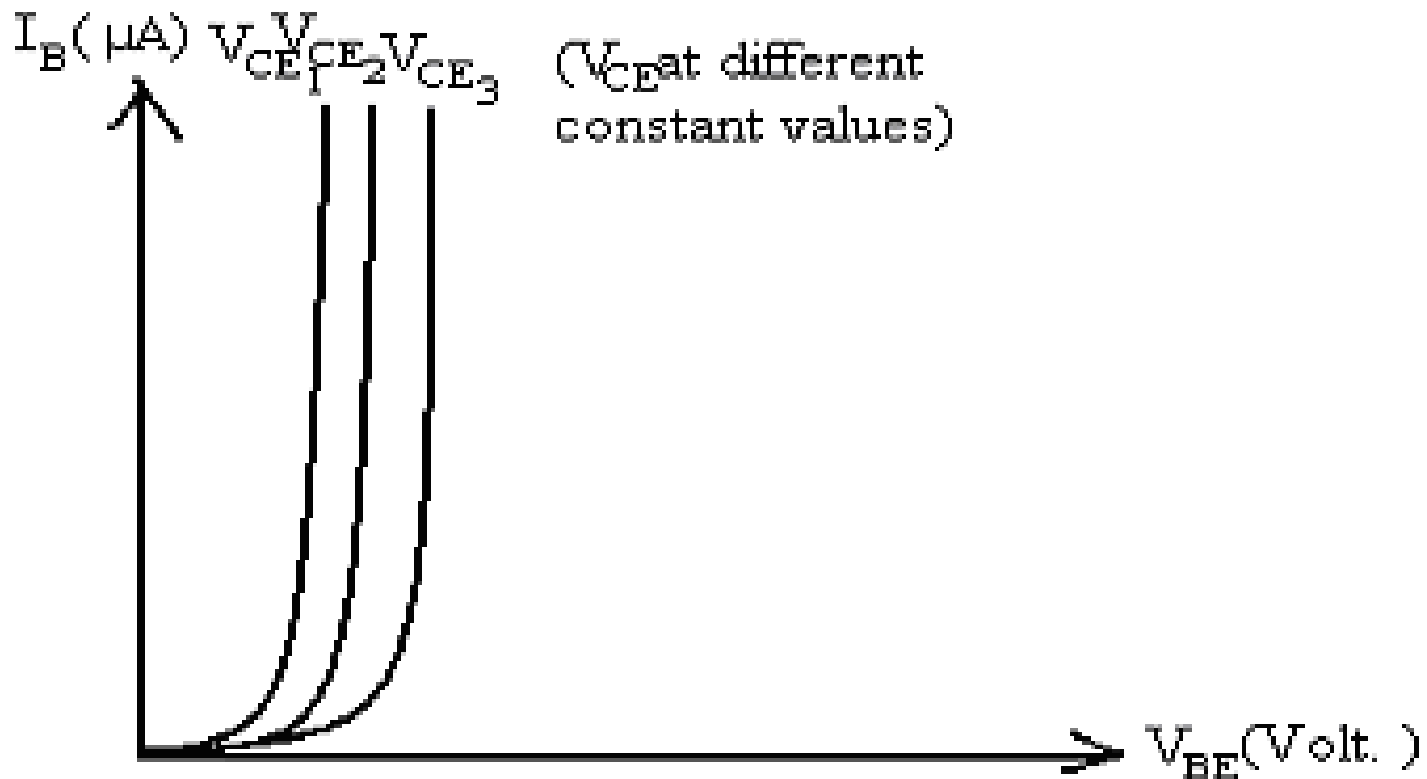
# Input VI Characteristics

It is the curve between the current  $I_B$  and voltage  $V_{BE}$  at constant collector base voltage  $V_{CE}$ .



# Output VI Characteristics

It is the curve between the current  $I_C$  and voltage  $V_{CE}$  at constant collector base voltage  $I_B$ .

